

# Practical integrator using operational amplifier

Russel Shawn Dsouza  
171EC143

Sathvik S Prabhu  
171EC146

- 1 Aim
- 2 Components required
- 3 Theory
- 4 Design
- 5 Calculations
- 6 Simulation
- 7 Waveforms
- 8 Observations
- 9 Result